



I added a rocker switch on the dash, but it could be a push switch. Either way, only the blinker flasher OR the hazard flasher can be powered at any given time. The diodes prevent the left and right blinker circuit from being connected at the output terminal of the hazard flasher.

Diodes. I used
PX6007. 6A, 1000v
SCRs